

- (1) A parallel-plate capacitor has circular plates of 8.20 cm radius and 1.30 mm separation.
 (a) Calculate the capacitance. (b) Find the charge for a potential difference of 120 V.

3. **THINK** The capacitance of a parallel-plate capacitor is given by $C = \epsilon_0 A/d$, where A is the area of each plate and d is the plate separation.

EXPRESS Since the plates are circular, the plate area is $A = \pi R^2$, where R is the radius of a plate. The charge on the positive plate is given by $q = CV$, where V is the potential difference across the plates.

ANALYZE (a) Substituting the values given, the capacitance is

$$C = \frac{\epsilon_0 \pi R^2}{d} = \frac{(8.85 \times 10^{-12} \text{ F/m}) \pi (8.2 \times 10^{-2} \text{ m})^2}{1.3 \times 10^{-3} \text{ m}} = 1.44 \times 10^{-10} \text{ F} = 144 \text{ pF}.$$

(b) Similarly, the charge on the plate when $V = 120 \text{ V}$ is

$$q = (1.44 \times 10^{-10} \text{ F})(120 \text{ V}) = 1.73 \times 10^{-8} \text{ C} = 17.3 \text{ nC}.$$

LEARN Capacitance depends only on geometric factors, namely, the plate area and plate separation.

- (2) The plates of a spherical capacitor have radii 38.0 mm and 40.0 mm. (a) Calculate the capacitance. (b) What must be the plate area of a parallel-plate capacitor with the same plate separation and capacitance?

$$C = 4\pi\epsilon_0 \frac{ab}{b-a} = \frac{(40.0 \text{ mm})(38.0 \text{ mm})}{(8.99 \times 10^9 \frac{\text{N}\cdot\text{m}^2}{\text{C}^2})(40.0 \text{ mm} - 38.0 \text{ mm})} = 84.5 \text{ pF}.$$

(b) Let the area required be A . Then $C = \epsilon_0 A/(b-a)$, or

$$A = \frac{C(b-a)}{\epsilon_0} = \frac{(84.5 \text{ pF})(40.0 \text{ mm} - 38.0 \text{ mm})}{(8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2)} = 191 \text{ cm}^2.$$

- (3) You have two flat metal plates, each of area 1.00 m^2 , with which to construct a parallel-plate capacitor. (a) If the capacitance of the device is to be 1.00 F , what must


be the separation between the plates? (b) Could this capacitor actually be constructed?

6. (a) We use $C = A\epsilon_0/d$. The distance between the plates is

$$d = \frac{A\epsilon_0}{C} = \frac{(1.00\text{ m}^2)(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)}{1.00\text{ F}} = 8.85 \times 10^{-12} \text{ m}.$$

(b) Since d is much less than the size of an atom ($\sim 10^{-10} \text{ m}$), this capacitor cannot be constructed.

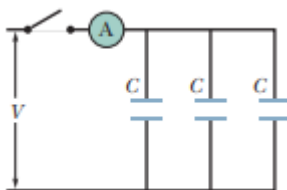
- (4) Each of the uncharged capacitors in Fig. has a capacitance of $25.0 \mu\text{F}$. A potential difference of $V = 4200 \text{ V}$ is established when the switch is closed. How many coulombs of charge then pass through meter A



The charge that passes through meter A is


$$q = C_{\text{eq}}V = 3CV = 3[25.0 \mu\text{F}][4200 \text{ V}] = 0.315 \text{ C}.$$

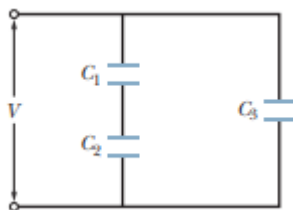- (5) In Fig. find the equivalent capacitance of the combination. Assume that C_1 is $10.0 \mu\text{F}$, C_2 is $5.00 \mu\text{F}$, and C_3 is $4.00 \mu\text{F}$.



$$C_{\text{eq}} = C_3 + \frac{C_1 C_2}{C_1 + C_2} = 4.00 \mu\text{F} + \frac{[10.0 \mu\text{F}][5.00 \mu\text{F}]}{10.0 \mu\text{F} + 5.00 \mu\text{F}} = 7.33 \mu\text{F}.$$

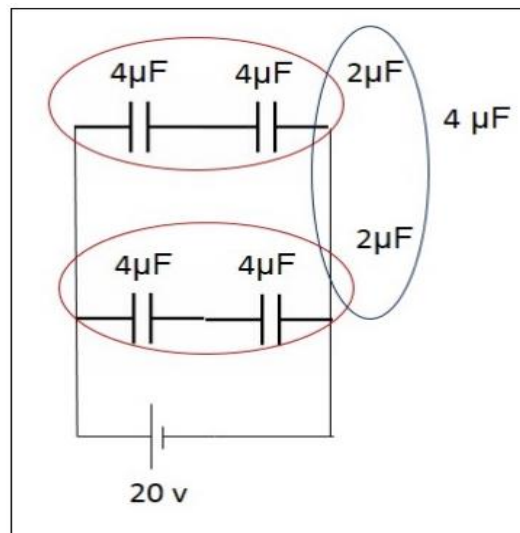- (6) Evaluate the circuit shown below to determine the effective capacitance and then the charge and voltage across each capacitor.



The equivalent capacitance is $4\mu\text{F}$. Voltage across the equivalent capacitor is 20 V

This voltage is also across both of the $2\mu\text{F}$ capacitors that were created by the series combinations in each branch.

Find the charge on each $2\mu\text{F}$ capacitor:

$$C = Q/V$$

$$2\mu\text{F} = Q/20$$

$$Q = 40\mu\text{C}$$

The $4\mu\text{F}$ capacitors in each branch have the same charge as the $2\mu\text{F}$ capacitors. Use this to find the voltage across each:


$$C = Q/V$$

$$4\mu\text{F} = 40\mu\text{C}/V$$

$$V = 10\text{ volts}$$

In summary, each of the original $4\mu\text{F}$ capacitors have a charge of $40\mu\text{C}$ and a voltage of 10 volts

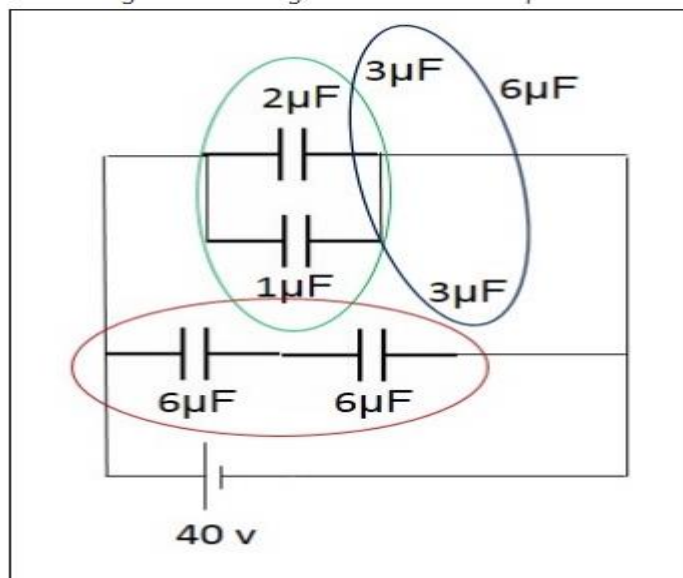- (7) Evaluate the circuit shown below to determine the effective capacitance and then the charge and voltage across each capacitor.



The equivalent capacitance is $6\mu\text{F}$. The voltage across the equivalent capacitance is 40V as is the voltage across the $3\mu\text{F}$ capacitors and is the same as the $1\mu\text{F}$ and $2\mu\text{F}$ capacitors.

Find the charge on the $1\mu\text{F}$ capacitor:

$$C = Q/V$$

$$1\mu\text{F} = Q/40$$

$$Q = 40\mu\text{C}$$

Find the charge on the $2\mu\text{F}$ capacitor:

$$C = Q/V$$

$$2\mu\text{F} = Q/40$$

$$Q = 80\mu\text{C}$$

Find the charge on the $3\mu\text{F}$ capacitors:

$$C = Q/V$$

$$3\mu\text{F} = Q/40$$

$$Q = 120\mu\text{C}$$

This is the same charge on each of the $6\mu\text{F}$ capacitors.

Find the voltage on each of the $6\mu\text{F}$ capacitors:

$$C = Q/V$$

$$6\mu\text{F} = 120\mu\text{C}/V$$

$$V = 20\text{V}$$